
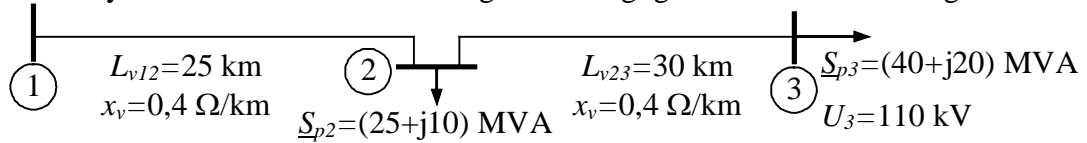


## ELEKTRIJADA 2008: ANALIZA ELEKTROENERGETSKIH SISTEMA

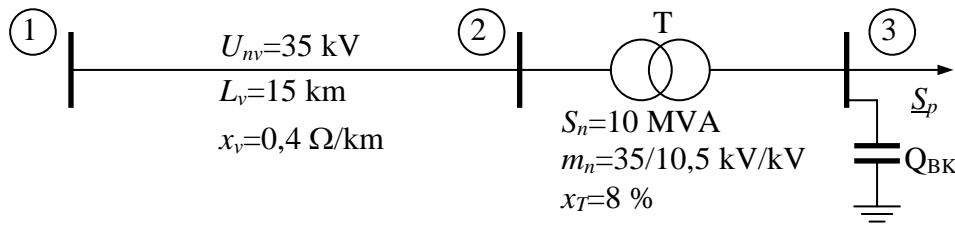- 1.** Power system are shown on the figure. Using given data find voltage at bus 1.




- 2.** Power system, shown on the figure, supply consumption area with constant power  $\underline{S}_p = (5 + j3)$  MVA. Voltage magnitude at bus 1 is  $U_1 = 36$  kV = const. With shunt capacitor bank on the bus 3 voltage magnitude at bus 3 is  $U_2 = 10,5$  kV. Find reactive power of shunt capacitor bank. Find system power losses before and after installation of shunt capacitor.



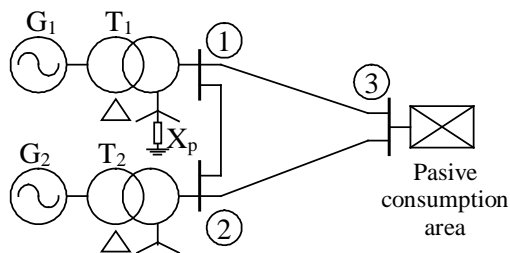- 3.** Simply power system is shown on the figure. In the case of single phase to ground fault at bus 1 find phase current on line with transformer  $T_2$ .

Voltage at bus 3 before fault was  $U_{1f} = 1$  r.j



System data are (p.u.):

$G_1 \equiv G_2:$	$X_d = X_i = 0,15$	$X_o = 0,05$
$T_1 \equiv T_2:$	$X_d = X_i = 0,05$	$X_o = 0,05$
$V_{12} \equiv V_{13} \equiv V_{23}:$	$X_d = X_i = 0,1$	$X_o = 0,3$
Reactor:	$X_p = 0,01$	

- 4.** For nesimetrical system are known:

$$\underline{I}_A + \underline{I}_B + \underline{I}_C = 1,0 \text{ r.j. } /240^\circ; \quad \underline{I}_B / \underline{I}_A = 1,0 \text{ r.j. } /120^\circ; \quad \underline{I}_C = 1,0 \text{ r.j. } /180^\circ.$$

Find current at phases A and B and all simetrical coponent. Draw current vector diagrams for all phases and symetrical systems.

- 5.** Simply power system is given on the figure. Find state variables after first iteration using Newton-Raphsons method for load flow calculation. Find power injection at buses 1 and 2 and power losses.

