

ELEKTRIJADA 2009 – Analiza EES-a

ANNOTATION: You must chose only one of given answers for problems. Right answers worth 1 point. Wrong answers worth -0.25 point. For answers “I don’t know” there is no negative points.

1. Line with parameters $X_g=10 \Omega$ i $R_g \approx 0 \Omega$. Is given. Voltage at beginning of line is $U_1=110$ kV, and power at the end of line is $S_2=(50+j30)$ MVA. Find voltage at the end of line U_2 . The answer is:

- a)
- b) $\underline{U}_2 = 107.1e^{-j2.43^\circ}$ kV
- c)
- d) No one of given answers
- e) I don’t now

2. Transmission line ($U_n=220$ kV, $f_n=50$ Hz) with parameters

$r_v=0,08 \Omega/\text{km}$,
 $l_v=1,2$ mH/km,
 $c_v=9,55$ nF/km,
 $L_v=100$ km,


is given. Voltage and power at the beginning of line are $U_l=220$ kV and $S_l=(100+j50)$ MVA. Using “ π ” model of line find power losses. The answer is:

- a) $\underline{S}_{\text{gub}}=(2.195-j3.35)$ MVA
- b) $\underline{S}_{\text{gub}}=(2.195+j10.343)$ MVA
- c) $\underline{S}_{\text{gub}}=(2.195+j3.35)$ MVA
- d) No one of given answers
- e) I don’t now

3. Bus A supplied consumption area with constant power $\underline{S}_p=(6+j4)$ MVA. Shunt capacitor bank with constant capacitance $C=60 \mu\text{F}/\text{phase}$ is connected at bus A. In that case voltage at bus A is $U_A=10.3$ kV. Find power factor at bus A. The answer is:

- a) $\cos \varphi_A=$
- b) $\cos \varphi_A=0.9487$
- c) $\cos \varphi_A=$
- d) No one of given answers
- e) I don’t now

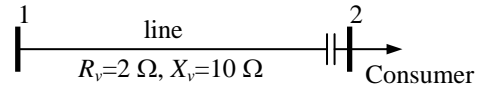
4. Transmission line, shown on the figure, supply consumption area with $\text{tg} \varphi_p=0.5$. Near bus 2 serial capacitor bank is connected. Find value of serial capacitor bank (X_c) which fully compensated voltage drop from bus 1 to bus 2.



The answer is:

- a)
- b)
- c) $X_c=14 \Omega$
- d) No one of given answers
- e) I don’t now

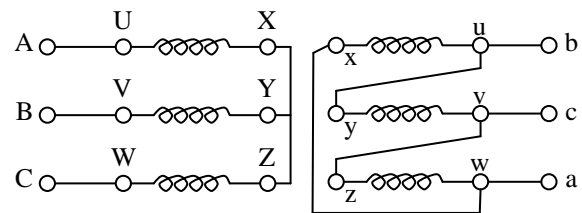5. For transformer, given at Figure, find phase group.




The answer is:

- a) 1
- b) 3
- c) 5
- d) No one of given answers
- e) I don’t now

6. Equivalent impedances for all three symmetrical systems at one bus are $\underline{Z}_i=jX$, $\underline{Z}_i=\underline{Z}_d$ i $\underline{Z}_o=jkX$. Find three phase fault and single phase to ground fault current ratio at the bus in function of parameter k. The answer is:

- a) $|\underline{I}_{3k}|/|\underline{I}_{1k}|=$
- b) $|\underline{I}_{3k}|/|\underline{I}_{1k}|=(2+k)/3$
- c) $|\underline{I}_{3k}|/|\underline{I}_{1k}|=$
- d) No one of given answers
- e) I don’t now

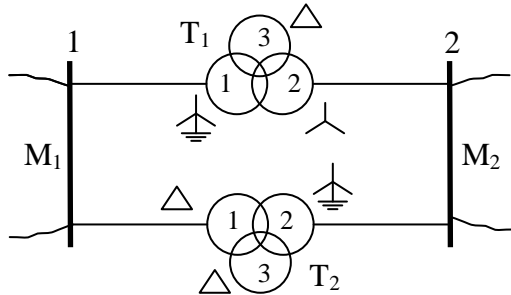
7. Two networks M_1 and M_2 are connected via two three wind transformer (see figure). Equivalent zero-sequence reactances for networks are $X_{0M1}=X_{0M2}=0.1$ r.j.. Transformers have same reactances for correspond windings $X_1=0.3$ r.j., $X_2=0.38$ r.j. and $X_3=0.2$ r.j.. Find equivalent zero-sequence from busses 1 i 2.



The answer is:

- a) $Z_{01}^{ekv}=j0.1$ r.j., $Z_{02}^{ekv}=j0.0833$ r.j.
- b) $Z_{01}^{ekv}=j0.0833$ r.j., $Z_{02}^{ekv}=j0.0833$ r.j.
- c) $Z_{01}^{ekv}=j0.0833$ r.j. $Z_{02}^{ekv}=j0.1$ r.j.
- d) No one of given answers
- e) I don't now

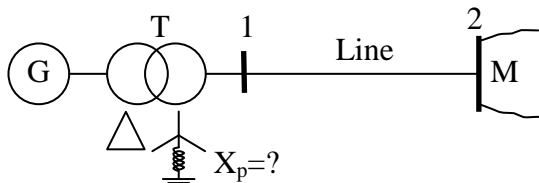8. Simply power system with data is shown on the figure.




G: $S_{nG}=200$ MVA, $U_{nG}=10.5$ kV, $x_g=20$ %
 T: $S_{nT}=S_{nG}$, $m_T=110/10.5$ kV/kV, $x_T=10$ %
 V: $x_{dv}=0.4$ Ω /km, $x_{ov}=3 \cdot x_{dv}$, $L_v=50$ km
 M: Mreža "∞" snage

Find value of reactor (X_p) which limits single phase to ground current at bus 1 at value 5.5 kA. The answer is:

- a)
- b) $X_p=5.016$ Ω
- c)
- d) No one of given answers
- e) I don't now

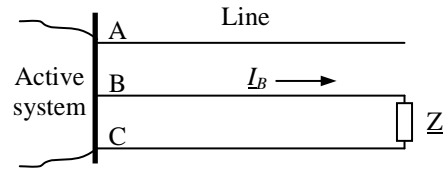9. Active network via three phase transmission line supply consumption Z (see figure). Current at phase B is $I_B = 3e^{-j120^\circ}$ r.j. Find symmetrical component for transmission line current



The answer is:

- a)
- b) $I_d = \sqrt{3}e^{-j30^\circ}$ r.j., $I_i = \sqrt{3}e^{j150^\circ}$ r.j., $I_0 = 0$ r.j.
- c)
- d) No one of given answers
- e) I don't now

10. In table data for busses in one transmission network (voltage, voltage angle, active and reactive generation and load power) are given. Data are given in p.u.

čv.	U	θ	P_G	P_P	Q_G	Q_P
1	1.05	0	/	1.2	/	1.0
2	/	/	0	1.0	0	0.5
3	1.00	/	2.1	0.8	/	0.4
4	1.02	/	2.4	1.0	/	0.3
5	/	/	0	1.0	0	0.4
6	/	/	0	1.5	0	0.8

Based on given data find dimension of Jacobian matrix in Newton-Raphson method for power flow calculation. The answer is:

- a) $\dim(J)=7 \times 7$
- b) $\dim(J)=5 \times 5$
- c) $\dim(J)=6 \times 6$
- d) No one of given answers
- e) I don't now